

Prelab assignment (to be completed before coming to Lab 5):

1. Read through the entire Lab 5 handout and Lab1 notes.
2. (10 points) Why is an isolation transformer required when using a Variac as a signal source? (hint: see Part I of the lab, and the Prelab notes)
3. (10 points) Why is a 10:1 isolation transformer required when using an oscilloscope to measure the output waveform of a bridge rectifier? (hint: see the Prelab notes)
4. (10 points) What does the “line trigger” do, and why will we use line triggering while measuring the output waveforms of our rectifier circuits supplied by the AC power mains? (hint: see Part I of the lab)
5. (10 points) Build the half wave rectifier circuit shown in Fig 5-1 in Pspice. Select a D1N4002 for D1. Set R2 = 1k $\Omega$  and C1 = 1nF. Add V1 as a sine source VSIN set for 10Vp at 60 Hz with no DC offset. Place two voltage probes for measuring Vin (V1), and Vo (at R2).

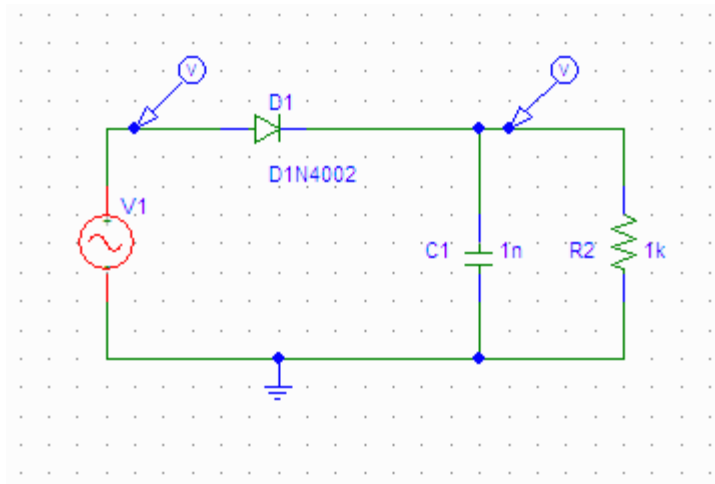


Figure 5-1

Use Pspice transient analysis to simulate the  $V_{in}(t)$  and  $V_o(t)$  waveforms from  $t = 0$  to  $t = 50\text{ms}$  in  $0.2\text{ms}$  steps. On the simulation results, use the cursors to find measure  $V_{in_{max}}$ ,  $V_{o_{min}}$ , and  $V_{o_{max}}$ . Calculate  $V_{opp} = V_{o_{max}} - V_{o_{min}}$  and  $V_D$  (the forward diode voltage drop =  $V_{in_{max}} - V_{o_{max}}$ ).

$V_{in_{max}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_,  $V_{pp} =$  \_\_\_\_\_,  $V_D =$  \_\_\_\_\_

Enter these values in Part I-2 on the Data sheet.

Place a label on the simulation with your name and “Prelab 5 Half Wave”, and print the simulation.

6. (25 points) Modify the Pspice model in question 5 by changing C1 to  $10\mu\text{F}$  and replacing R2 with a variable resistor. Run a Parametric Sweep analysis for  $R_L = 500\Omega$  to  $10500\Omega$  in  $2000\Omega$  steps. Use the cursor to measure and mark  $V_{o_{min}}$  for  $R_L = 500, 2500,$  and  $10500$  and  $V_{o_{max}}$  (note:  $V_{o_{max}}$  does not change much as  $R_L$  varies, so measure and mark  $V_{o_{max}}$  for only one resistor value).

Calculate  $V_{opp}$  for three values of  $R_L$ .

$R_L = 500\Omega$   $V_{o_{min}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_  $V_{pp} =$  \_\_\_\_\_

$R_L = 2500\Omega$   $V_{o_{min}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_  $V_{pp} =$  \_\_\_\_\_

$R_L = 10500\Omega$   $V_{o_{min}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_  $V_{pp} =$  \_\_\_\_\_

Enter these results in Part I-3 on the Data sheet.

Edit the bottom right drawing information box to include our name, the date, and “Prelab 5 Half Wave”. Save the schematic and then print it.

Place a label on the simulation with your name and “Prelab 5 Half Wave”, and print the simulation. On the print, write the resistor value at each minimum voltage that has a simulation label, and write  $V_{max}$  at the max voltage simulation label.

7. (25 points) Edit the half wave rectifier of question 6 to build the full wave bridge rectifier circuit shown in Fig 5-2.

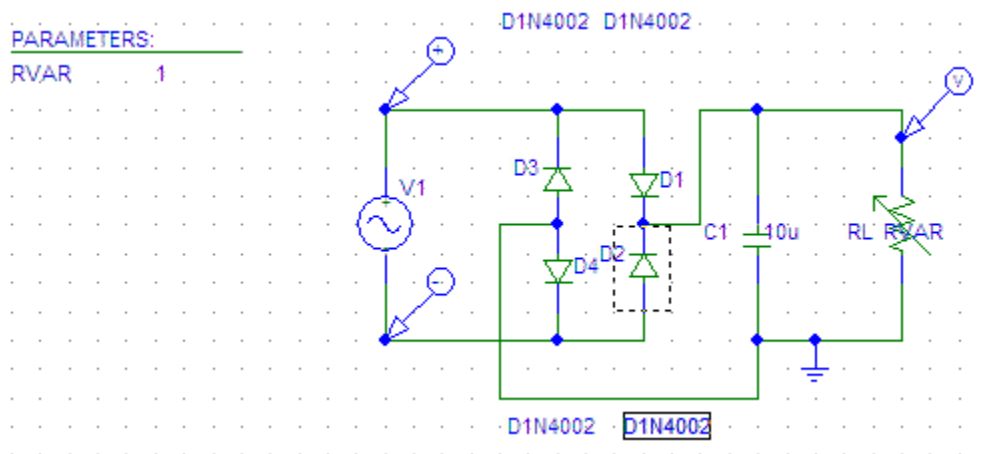


Figure 5-2

Note: You must use a differential voltage probe to measure V1 because V1 is not grounded.

Run the same parametric sweep that you did on question 6.

Use the cursor to measure and mark  $V_{o_{\min}}$  for  $R_L = 500, 2500,$  and  $10500$  and  $V_{o_{\max}}$  (note:  $V_{o_{\max}}$  does not change much as  $R_L$  varies, so measure and mark  $V_{o_{\max}}$  for only one resistor value).

Calculate  $V_{pp} = V_{o_{\max}} - V_{o_{\min}}$  for three values of  $R_L$ .

$R_L = 500\Omega$   $V_{o_{\min}} =$  \_\_\_\_\_,  $V_{o_{\max}} =$  \_\_\_\_\_  $V_{Vpp} =$  \_\_\_\_\_

$R_L = 2500\Omega$   $V_{o_{\min}} =$  \_\_\_\_\_,  $V_{o_{\max}} =$  \_\_\_\_\_  $V_{Vpp} =$  \_\_\_\_\_

$R_L = 10500\Omega$   $V_{o_{\min}} =$  \_\_\_\_\_,  $V_{o_{\max}} =$  \_\_\_\_\_  $V_{Vpp} =$  \_\_\_\_\_

Enter these results in Part II-3 on the Data sheet.

Edit the bottom right drawing information box to include our name, the date, and “Prelab 5 Full Wave”. Save the schematic and then print it.


Place a label on the simulation with your name and “Prelab 5 Full Wave”, and print the simulation. On the print, write the resistor value at each minimum voltage that has a simulation label, and write  $V_{\max}$  at the max voltage simulation label.

8. (5 points) Look at the Parametric sweep results for the full wave and half wave circuits. Compare  $V_{o_{\max}}$ ,  $V_{o_{\min}}$ , and  $V_{pp}$  for the three resistor values. What can you say about the output voltage as  $R_L$  decreases?
  
  
  
  
  
  
  
  
  
  
9. (5 points) Which rectifier circuit provides the best regulation (lowest ripple)? Why is this?

**This page left blank for calculations**

**Part I: Half Wave Rectifier and Filter**

1. Build the rectifier circuit of Figure 5-3 on the protoboard. D1 is a 1N4001, 1N4002, or 1N4003 rectifier. Use the decade resistor for  $R_L$  and leave C1 out of the circuit.

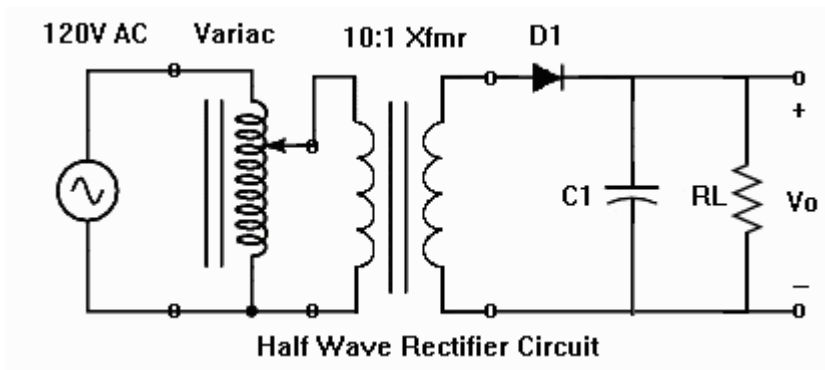

**Figure 5-3**



For  $V_{in}$ , use the Variac autotransformer and 10:1 isolation transformer for the input voltage source. The Variac plugs into the 120V AC bench power outlet. The red isolation transformer plugs into the autotransformer output.

**Note:** The isolation 10:1 step-down transformer must be used with the Variac to eliminate the possibility of hazardous voltages in your circuit and to safely isolate the power line from you and your circuit.

**Note:** Set your load resistor to 10.5k $\Omega$  before connecting the transformer to the rectifier circuit.

With the load resistor set to 10.5k $\Omega$  (10,500 $\Omega$ ), use banana leads to connect the isolation transformer output to the rectifier AC input.

Connect the scope to the isolation transformer and adjust the autotransformer until scope measures isolation transformer output to be 20Vpp. When the voltage has been set, move the scope connection to  $R_L$

2. **Set the scope trigger source to LINE** (using the Trigger EDGE button). Line triggering is used to synchronize the output waveforms to the 60Hz AC power line. Line triggering enables you to align and overlay the diode output waveforms for various load conditions by always beginning the trace at the AC power line 0V crossover. **Do not use the “autoscale” button** for any rectifier measurements.

Set the Horizontal scale to 5ms/div, move the scope probe to  $R_L$  to **display the  $V_o$  waveform** on CH1 using DC input coupling, and measure the maximum, minimum, and ripple (peak-to-peak) load voltages. Calculate  $V_D$ . Record these values on the data sheet.

Use the computer to capture and save the DC coupled  $V_o$  waveform data  
Filename=\_\_\_\_\_ .txt

3. Connect a  $10\mu\text{f}$  filter capacitor (for C1) in parallel with  $R_L$ . Leave the Horizontal scale at  $5\text{ms/div}$  for all measurements and Display the  $V_o$  waveform on CH1. For each value of  $R_L$  in the table below, measure the DC coupled minimum, maximum, RMS, and peak-to-peak voltages, and calculate the diode forward voltage drop ( $V_D = V_{in_{max}} - V_{max}$ ). As  $R_L$  changes, you will need to **adjust the Vertical scale and position** to keep the waveform on the screen and large enough for quick measure to accurately find the voltages. **DO NOT USE AUTOSCALE!** Leave the horizontal scale at  $5\text{ms/div}$  for these measurements. Capture the DC coupled waveforms for  $R_L = 500\Omega$ ,  $2.5\text{k}\Omega$ , and  $10.5\text{k}\Omega$ . Record your measurements and calculations on the data sheet.
4. Use the buffer to overlay the  $500\Omega$  and  $2.5\text{k}\Omega$  waveforms and save the overlay.  
\_\_\_\_\_ .txt

Overlay the  $10.5\text{k}\Omega$ /no capacitor halfwave waveform (from # 2) with the  $10.5\text{k}\Omega/10\mu\text{f}$  waveform obtained in the table above. \_\_\_\_\_ .txt

Combine (overlay) the  $500\Omega/2.5\text{k}\Omega$  overlay with the  $10.5\text{k}\Omega$  overlay and save this composite overlay (there should be 4 traces in this composite). \_\_\_\_\_ .txt

Return to the main buffer and save the composite overlay as a jpeg file.

**\*Print one copy of the jpeg**, title the print, clearly identify the traces for each of the load conditions, write all names on the print, and attach the print to one of the lab reports.

**\*Answer the questions** on the data sheet.

## Part II: Full Wave Bridge Rectifier and Filter

1. Build the rectifier circuit of Figure 5-3 on the protoboard. Use the decade resistor for  $R_L$  and leave C1 out of the circuit.

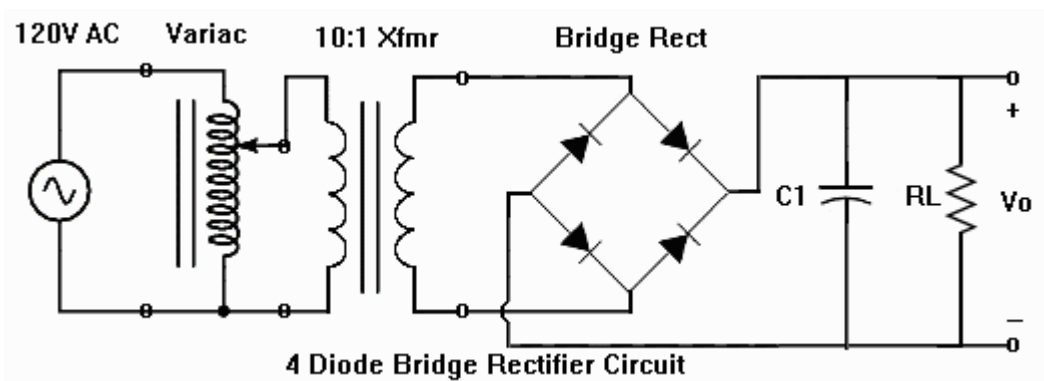


Figure 5-4

Use the same Variac/isolation transformer source that you used for the half wave rectifier.

With the load resistor set to  $10.5\text{k}\Omega$  ( $10,500\Omega$ ), use banana leads to connect the isolation transformer output to the rectifier AC input. Connect the scope to the isolation transformer and

adjust the autotransformer until scope measures isolation transformer output to be 20Vpp. When the voltage has been set, move the scope connection to  $R_L$

2. **Set the scope trigger source to LINE and the horizontal scale to 5ms/div.**

Display the  $V_o$  waveform on CH1 using DC input coupling and measure the minimum, maximum, RMS, and peak-to-peak voltages. Calculate  $V_D$ . Record these values on the data sheet. Record these measurements on the data sheet.

Use the computer to capture and save the DC coupled  $V_o$  waveform data  
Filename=\_\_\_\_\_ .txt

3. Connect a 10 $\mu$ f filter capacitor in parallel with  $R_L$ . Display the  $V_o$  waveform on CH1. For the values of  $R_L$  in the table below, measure the DC coupled maximum, minimum, and peak-to-peak voltages, and calculate the diode forward voltage drop ( $V_D = V_{in_{max}} - V_{max}$ ). Remember that there are two diodes conducting, so  $V_D$  will be half of the difference between  $V_{max}$  and 10V. As  $R_L$  changes, you will need to adjust the Vertical scale and position to keep the waveform on the screen and large enough for quick measure to accurately find the voltages. DO NOT USE AUTOSCALE! Record the measurements and calculations on the data sheet.

Capture the DC coupled waveforms for  $R_L = 500\Omega, 2.5k\Omega, \text{ and } 10.5k\Omega$ .

4. Use the buffer to overlay the 500 $\Omega$  and 2.5K $\Omega$  waveforms and save the overlay.  
\_\_\_\_\_ .txt

Overlay the 10.5k $\Omega$ /no capacitor fullwave waveform (from the previous page) with the 10.5k $\Omega$ /10 $\mu$ f waveform obtained in the table above. \_\_\_\_\_ .txt

Overlay (combine) the 500 $\Omega$ /2.5K $\Omega$  overlay and the 10.5k $\Omega$  overlay and save this composite overlay (there should be 4 traces in this composite). \_\_\_\_\_ .txt

Return to the main buffer and save the composite overlay as a jpeg file.

**\*Print one copy of the jpeg**, title the print, identify the traces for each of the load conditions, write all partners names on the print, and attach the print to one of the lab reports.

**\*Answer the questions on the data sheet.**

5. **Before you leave:** Shut down Windows, return cables to racks, return parts to correct drawer bins, return adapters to container, turn off bench power, clear bench, and place seat under bench.  
**(Counts as 5 points of the Lab grade)**

(100 points total)

100 points total)

Names:

by first name: \_\_\_\_\_  
 2<sup>nd</sup> alphabetically – wiring    3<sup>rd</sup> alphabetically – Labview    1<sup>st</sup> alphabetically – data sheet

**Part I: Half Wave Rectifier and Filter**

2. From the Prelab Pspice simulations:

$V_{in_{max}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_,  $V_{pp} =$  \_\_\_\_\_  $V_D =$  \_\_\_\_\_

Measured in the Lab:

$V_{in_{max}} =$  \_\_\_\_\_,  $V_{o_{max}} =$  \_\_\_\_\_,  $V_{pp} =$  \_\_\_\_\_  $V_D =$  \_\_\_\_\_

3. From the Prelab Pspice simulations:

<b><u>RL Ω</u></b>	<b><u>Vmin</u></b>	<b><u>Vmax</u></b>	<b><u>Vpp</u></b>
500	_____	_____	_____
2.5k	_____	_____	_____
10.5k	_____	_____	_____

Measured in the Lab:

<b><u>RL Ω</u></b>	<b><u>Vmin</u></b>	<b><u>Vmax</u></b>	<b><u>Vpp</u></b>	<b><u>Vrms</u></b>	<b><u>Data filename</u></b>
500	_____	_____	_____	_____	_____ .txt
2.5k	_____	_____	_____	_____	_____ .txt
10.5k	_____	_____	_____	_____	_____ .txt
∞	_____	_____	_____	_____	do not capture

4. What changes do you see in  $V_{max}$ ,  $V_{min}$ ,  $V_{rms}$ , and the ripple ( $V_{pp}$ ) as  $R_L$  changes?

What is responsible for these changes? (hint: see prelab notes)

How do the voltages compare to the values predicted by Pspice? What accounts for the difference?

**Part II: Full Wave Bridge Rectifier and Filter**

2. Measured in the Lab:

$V_{in\_max} =$  \_\_\_\_\_,  $V_{o\_max} =$  \_\_\_\_\_,  $V_{pp} =$  \_\_\_\_\_  $V_D =$  \_\_\_\_\_

3. From the Prelab Pspice simulations:

$R_L \Omega$	Vmin	Vmax	Vpp
500	_____	_____	_____
2.5k	_____	_____	_____
10.5k	_____	_____	_____

Measured in the Lab:

$R_L \Omega$	Vmin	Vmax	Vpp	Vrms	Data filename
500	_____	_____	_____	_____	_____ .txt
2.5k	_____	_____	_____	_____	_____ .txt
10.5k	_____	_____	_____	_____	_____ .txt
$\infty$	_____	_____	_____	_____	do not capture

4. What changes do you see in  $V_{max}$ ,  $V_{min}$ ,  $V_{rms}$ , and the ripple ( $V_{pp}$ ) as  $R_L$  changes?

What is responsible for these changes? (hint: see prelab notes)

How do the voltages compare to the values predicted by Pspice? What accounts for the difference?

